2024 超大型積體電路電腦輔助設計概論


2024 Introduction to VLSI CAD Lab 9

學號:E14102305 姓名:簡笠恩


※作業要求的圖請使用電腦截圖程式截取,請勿用手機拍照的方式繳交 ※Report 檔請以 pdf 的格式繳交

A. NAND

 - 1. Presim
 - i. 請截取 terminal 顯示 job concluded 的圖



ii. 請截取 WaveView 中的波形

 


2. Post-sim


i. 請截取 terminal 顯示 job concluded 的圖


```
140.116.156.6 - PuTTY
                                                                         fontPath(SPS FONT PATH) = /usr/cad/synopsys/laker/cur/TTFont
Feature "Laker_L3_Plus" checked out successfully (Elapsed Time: 20.12s)
[1]
      Done
vlsicad6:/home/user2/vlsi24/vlsi2416 % vim circuit.sp
lsicad6:/home/user2/vlsi24/vlsi2416 % vim circuit.spi
vlsicad6:/home/user2/vlsi24/vlsi2416 % cd VLSI
lsicad6:/home/user2/vlsi24/vlsi2416/VLSI % cd VLSI
rlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI % cd Lab8
rlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % vim circuit.spi
lsicad6:/home/user2/vlsi24/vlsi24l6/VLSI/VLSI/Lab8 % vim testbench.sp
rlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % vim nand.pex.netlist
lsicad6:/home/user2/vlsi24/vlsi24l6/VLSI/VLSI/Lab8 % vim testbench.sp
lsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % hspice testbench.sp -o pos
Using: /usr/cad/synopsys/hspice/cur/hspice/linux64/hspice 'testbench.sp' -o pos
Warning(s) associated with encrypted block(s) were suppressed due to encrypted c
ontent.
               ***** hspice job concluded
>info:
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % wv &
[3] 28675
lsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 %
```

ii. 請截取 WaveView 中的波形

 


iii. DRC/LVS 結果

 

 

iv. Layout 截圖

 


3. 嘗試簡單說明 Presim 與 Post-sim 結果比較

可以發現我們 pre-sim 和 post-sim 的結果是相像的,這是因

為我們 pre-sim 是以參數去模擬我們的電路,而 layout 就是 將真實樣貌畫在 board 上。所以結果相像我認為是應該的。

B. NOR

 - 1. Presim
 - i. 請截取 terminal 顯示 job concluded 的圖



ii. 請截取 WaveView 中的波形




2. Post-sim


i. 請截取 terminal 顯示 job concluded 的圖


```
140.116.156.6 - PuTTY
                                                                            ×
Using: /usr/cad/synopsys/hspice/cur/hspice/linux64/hspice 'testbench.sp' -o pos
               ***** hspice job concluded
>info:
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % wx &
[3] 6746
wx: Command not found.
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 %
[3]
      Exit 1
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % vim circuit.spi
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % vim testbench.sp
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % vim nor.pex.netlist
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % vim testbench.sp
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % hspice testbench.sp -o pos
Using: /usr/cad/synopsys/hspice/cur/hspice/linux64/hspice 'testbench.sp' -o pos
Warning(s) associated with encrypted block(s) were suppressed due to encrypted c
ontent.
>info: ***** hspice job concluded
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 % wv &
[3] 28728
vlsicad6:/home/user2/vlsi24/vlsi2416/VLSI/VLSI/Lab8 %
```

ii. 請截取 WaveView 中的波形

 


iii. DRC/LVS 結果

 

 

iv. Layout 截圖

 

- 3. 嘗試簡單說明 Presim 與 Post-sim 結果比較
- C. 可以發現我們 pre-sim 和 post-sim 的結果是相像的,這是因為我們 pre-sim 是以參數去模擬我們的電路,而 layout 就是將真實樣 貌畫在 board 上。所以結果相像我認為是應該的。

D. 心得討論

這次 lab 是第一次畫 layout,我是從 inverter 先下手的,一開始沒有熟記裡面的規則可以說是碰到重重困難,還好的是什麼沒有,我的耐心和時間巨多,所以在我努力不懈下,我順利地畫完inverter 而有了這個經驗後,我在畫這次 lab 時就非常順利的完成了。