National Cheng Kung University Department of Electrical Engineering

Introduction to VLSI CAD (Spring 2024)

Lab Session 4

Register Files, Manhattan Distance and LFSR

Name	Student ID	
簡笠恩	E14102305	
Practical Sections	Points	Marks
Prob A	30	
Prob B	30	
Prob C	20	
Report	15	
File hierarchy, namingetc.	5	
Notes:	•	

Due Date: 15:00, March 27, 2024 @ moodle

Deliverables

- 1) All Verilog codes including testbenches for each problem should be uploaded. NOTE: Please **DO NOT** include source code in the paper report!
- 2) All homework requirements should be uploaded in this file hierarchy or you will not get the full credit.
 - NOTE: Please DO NOT upload waveforms!
- 3) Important! TA will use the command in Appendix A to check your design under SoC Lab environment, if your code can not be recompiled by TA successfully using the commands, you will not get the full credit.
- 4) If you upload a dead body which we can't even compile you will get NO credit!
- 5) All Verilog file should get at least 90% superLint Coverage.
- 6) File hierarchy should not be changed; it may cause your code can not be recompiled by TA successfully using the autograding commands


 


Fig.1 File hierarchy for Homework submission

Prob A: SIPO Register File

 

- 1. Based on the SIPO register file structure in LabA, please design a 128 x 32 SIPO register file with 5 output ports.
- 2. Port list

Signal	Туре	Bits	Description	
clk	input	1	clock	
rst	input	1	reset	
reg_enable	input	1	register file enable	
reg_write	input	1	$0 \rightarrow \text{read } 1 \rightarrow \text{write}$	
src_addr	input	7	source address	
write_addr	input	7	write address	
write_data	input	32	write data	
src1	output	32	read data source1	
src2	output	32	read data source2	
src3	output	32	read data source3	
src4	output	32	read data source4	
src5	output	32	read data source5	

3. Show the simulation result on the terminal.


4. Show waveforms to explain that your register work correctly when read and write.



從此圖可知 reg_write = 0 為 read 模式故


我們第一個要讀的是 69 暫存器所以 src1 為其內的值,後面四個為 6a,6b,6c,6d 的值,src5 會是 69 結尾,如圖所示,前面四個也是如此。

5. Show SuperLint coverage

 

1 - 2/69 = 97%

Prob B: Finding Smallest Distance

 

1. Please design a circuit that will find the smallest distance between the input feature and input colors, based on the structure given in the LAB4 slide.

2. Port listManhattan:


Signal	Туре	Bits	Description
clk	input	1	Clock pin.
rst	input	1	Reset pin.
clear	input	1	Set all registers to 0.
c_en	input	1	Write compared colors enable. When c_en is high, then c_in0~7 is available.
if_en	input	1	Write input pixel enable. When if_en is high,

Min:

Signal	Туре	Bits	Description
d_0~7	input	10 each	Input data.
out_index	output	3	Output index.
out_distance	output	10	Output minimum distance.


3. Show the simulation result on the terminal.

 4. Show waveforms to explain that your design works correctly.



我們已第一題來說,當在 c_en 升起,會將每個 c_in 的值存入自製暫存器,而 input_feature 也是如此,且在他們值有變化時 temp 就會去計算他們之間的最小路徑的 3 個 part(RGB)並存在 temp 裡,然後會在時脈正源時,將 temp 的 RGB 相加存入個別的 d 裡,並且送入 min 裡判斷最小值是誰,最後將最小值送回去 output_distance 裡,並且判斷他是哪個 C_in。

5. Show SuperLint coverage

 

1-8/78+126+53 = 96.89%

Prob C: LFSR

1. Please design an 8-bit-LFSR, with the given feedback function in the LAB4 slide.


2. Port list

Signal	Туре	Bits	Description
clk	input	1	Clock pin.
rst	input	1	Reset pin. Reset all of the flip flops to zeros.
seed_val	input	1	the flip flops take seed as the initial state. the flip flops works as linear feedback shift register.
seed	input	8	Initial state value of LFSR.
d	output	8	Output value of LFSR

3. Feedback function

$d[0] = (d[7] \wedge d[5]) \wedge (d[4] \wedge d[2])$

 4. Show waveforms to explain that your LFSR module works correctly.




在 seed_val=1 時,會將 output d 存入 seed 值故為 7,在下一個時脈正源,因為 seed_val=0,故開始線性回饋,起始 7 為 8′b00000111,經過線性 $F \rightarrow d[0] = (0^0)^0(0^1) \rightarrow 0^1 \rightarrow 1$,故會變成 8′b00001111 即為 0f。

5. Show the simulation result on the terminal.

```
140.116.156.10 - PuTTY
                                                                    X
          Congratulations !!
       ** Simulation PASS!!
                               * *
$finish called from file "LFSR_tb.v", line 54.
$finish at simulation time
                                     259000
         VCS Simulation Report
Time: 2590000 ps
CPU Time: 0.660 seconds;
                                Data structure size: 0.0Mb
Fri Mar 22 10:32:22 2024
CPU time: .551 seconds to compile + .574 seconds to elab + .439 seconds to link
+ .704 seconds in simulation
vlsicad9:/home/user2/vlsi24/vlsi2416/Lab4 El4102305/ProbC % jg -superlint superl
JasperGold Apps 2018.03p001 64 bits 2018.04.24 18:13:05 PDT
```

6. Show SuperLint coverage

 

At last, please write the lesson you learned from Lab4

我覺得學到了關於 sequential 的寫法,且更了解暫存器的運作,還有 non-blocking 與 blocking 的區別,還有 for 迴圈的運用會使得程式較為簡化。 老話一句,好課一生推。

Appendix A : Commands we will use to check your homework

Problem		Command
2 1 4	Compile	% vcs -R regfile_sipo.v -full64
Prob A	Simulate	% vcs -R regfile_sipo_tb.v -debug_access+all -full64 +define+FSDB
Prob B	Compile	% vcs -R top.v -full64
	Simulate	% vcs -R top_tb.v -debug_access+all -full64 +define+FSDB
Prob C	Compile	% vcs -R LFSR.v -full64
	Simulate	% vcs -R LFSR_tb.v -debug_access+all -full64 +define+FSDB